

Total No. of Printed Pages—5

5 SEM TDC PHY M 4

2 0 1 6

(November)

PHYSICS

(Major)

Course : 504

(**Electronics**)

Full Marks : 60

Pass Marks : 24 (Backlog) / 18 (2014 onwards)

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Answer the following as directed : $1 \times 6 = 6$

(a) The ratio of $I_{r.m.s.}$ and $I_{d.c.}$ of a full-wave rectifier is

(i) 0.48

(ii) 1.11

(iii) 1.21

(iv) 1.57

(Choose the correct answer)

(b) The probability of occupancy of the Fermi level at room temperature is

~~(i)~~ 100%

(ii) 0%

~~(iii)~~ 50%

(iv) 75%

(Choose the correct answer)

(c) Which of the following specifications is not correct for a common-collector amplifier?

(i) High-input impedance

~~(ii)~~ Low-output impedance

(iii) High-voltage gain

(iv) High-current gain

(Choose the correct answer)

(d) What is the maximum theoretical efficiency of a class B push-pull transistor power amplifier?

(e) Crystal oscillators are superior to L - C oscillators mainly because of their

(i) small crystal size

(ii) wide frequency range

(iii) high value of Q

(iv) better frequency stability

(Choose the correct answer)

(f) What is the minimum number of gates required to implement the logic operation $X + \bar{X}Y$?

2. Answer the following questions : $2 \times 6 = 12$

(a) Intrinsic resistivity of silicon at 27°C is $2.8 \times 10^3 \Omega\text{-m}$. If the hole and electron mobilities are $0.18 \text{ m}^2\text{V}^{-1}\text{s}^{-1}$ and $0.38 \text{ m}^2\text{V}^{-1}\text{s}^{-1}$, calculate the intrinsic carrier density of silicon.

(b) What is meant by mobility of a carrier? How does it depend upon temperature and doping concentration?

(c) Distinguish between class A and class B amplifiers.

(d) An amplifier with negative feedback gives an output of 12.5 V with an input of 1.5 V . If the feedback is removed, the same output can be obtained for an input of 0.25 V . Calculate the feedback fraction.

(e) Show how an OP-AMP can be used as an integrator.

(f) Simplify the following Boolean equation :

$$X = (A + \bar{B})(B + C)B$$

3. (a) Why do the energy levels of an atom become energy bands in a solid? Sketch the energy band picture for. (i) an intrinsic. (ii) an n -type and (iii) a p -type semiconductor indicating the positions of the Fermi level, the donor or the acceptor levels. Distinguish between drift current and diffusion current in a semiconductor. $2+3+2=7$

(b) Explain the terms 'barrier potential' and 'depletion region' as applied to a p - n junction. Plot and explain the I - V characteristic of a junction diode. Also write an expression for diode current. $3+3+1=7$

Or

Discuss the two mechanisms of junction breakdown. Draw the circuit diagram of a d.c. power supply and explain the action of Zener diode as voltage regulator. $3+1+3=7$

4. (a) What is non-linear distortion? Mention any two methods of minimizing it. $1+2=3$

(b) What is transistor biasing? Discuss the base resistor method of biasing. What are its advantages and disadvantages? $1+3+2=6$

Or

Write down the hybrid equations of a transistor and define the h -parameters. What are the advantages of using the h -parameters? 1+3+2=6

5. (a) Explain the principle of operation of Wien bridge oscillator and find an expression for the frequency of oscillation. 5
- (b) Discuss briefly the steps involved in fabricating a monolithic integrated circuit. 4
6. (a) Draw the logic diagram of a full adder. Write the Boolean expressions for sum and carry, and give its truth table. 2+1+2=5
- (b) Establish that the NAND gate is a universal gate. 2
- (c) Use K-map to simplify the following Boolean expression : 2
- $$X = \bar{A}B + \bar{A}\bar{B}\bar{C} + AB\bar{C} + A\bar{B}\bar{C}$$
- (d) Draw a logic diagram for implementation of $Y = A\bar{B} + B\bar{A}$. 1